

# **Virginia Tech Research on Power Electronics for Fuel Cells**

**Jih-Sheng (Jason) Lai**  
**Virginia Polytechnic Institute and State  
University**

**August 8 – 9, 2002**  
**Presented at**

**Power Electronics for Fuel Cells Workshop**  
**National Fuel Cell Research Center**  
**University of California**  
**Irvine, California**

# Outline

- **Energy Management Issues**
- **Non-isolated Bidirectional DC/DC Converter for Fuel Cell Energy Management**
- **Isolated Bidirectional DC/DC converter for Fuel Cell Energy Management**
- **2001 Future Energy Challenge – Single-Phase 10-kW Fuel Cell Inverter**
- **Discussions**

# Why Fuel Cells Need **Auxiliary** Energy Source or Energy Storage?

- For **standalone** power supplies: need energy storage for load transient
- For **grid-connected** power supplies: need auxiliary energy source for start-up
- For all systems: need auxiliary energy source to provide power for control signals

# Problems of a Fuel Cell System without Energy Storage

- Fuel cell does not have storage capability
- Slow response, output voltage fluctuates with loads
- Source may not be continuously available
- Size (or capacity) needs to be higher than the peak load
- When sized enough for the maximum load, excess **energy will be wasted**


# **Energy Management with Energy Storages**

- **Optimum energy usage control**
- **Start-up control**
- **Load transient control**
- **Charging and discharging (bi-directional) controls for auxiliary energy storages**

# Design Considerations for Hybrid-Source Systems

1. **Utilization** of Primary Source
2. **Simple Power Circuit** (as simple as possible)
3. Voltage ratio
4. **Isolation** Requirement
5. **Energy Storage** Requirement
6. Inverter **DC Bus Voltage** Requirement
7. **Cost**
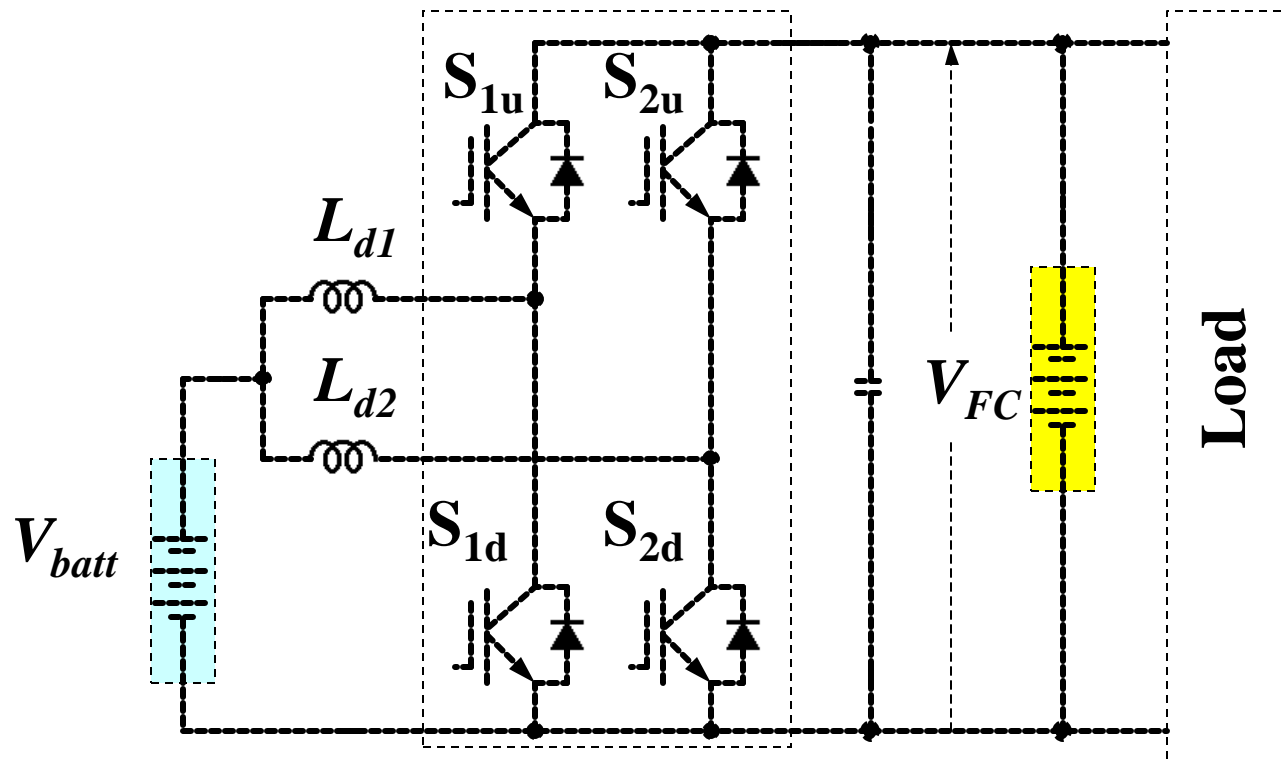
# Non-isolated **Bidirectional** DC/DC Converter for Fuel Cell Energy Management



Interleaved operation for both boost and buck modes →


- smaller passive components;
- less battery ripple current

# An Example of **Bi-Directional** DC-DC Converter with Interleaved Control


- LV side battery voltage range: 140 – 240 V
- HV side fuel cell voltage range: 250 – 425 V, nominal: 300 V
- HV DC bus voltage is unregulated
- Fuel cell power: up to 60 kW
- Battery power: up to 20 kW
- Load power level: up to 80 kW
- HV DC bus voltage is unregulated

# Battery and Fuel Cell Current Responses

from 60 kW to 80 kW Step Load Jump

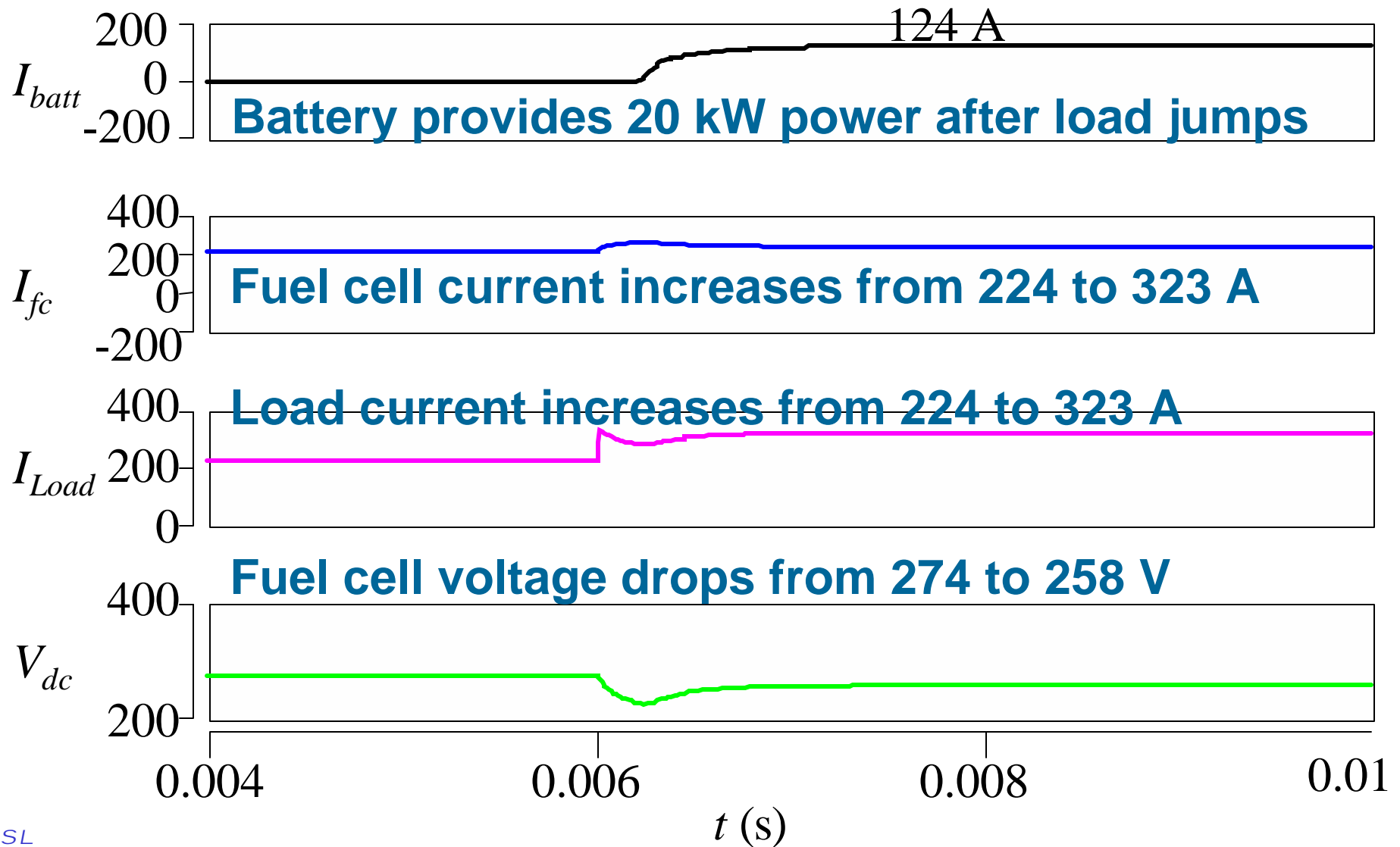

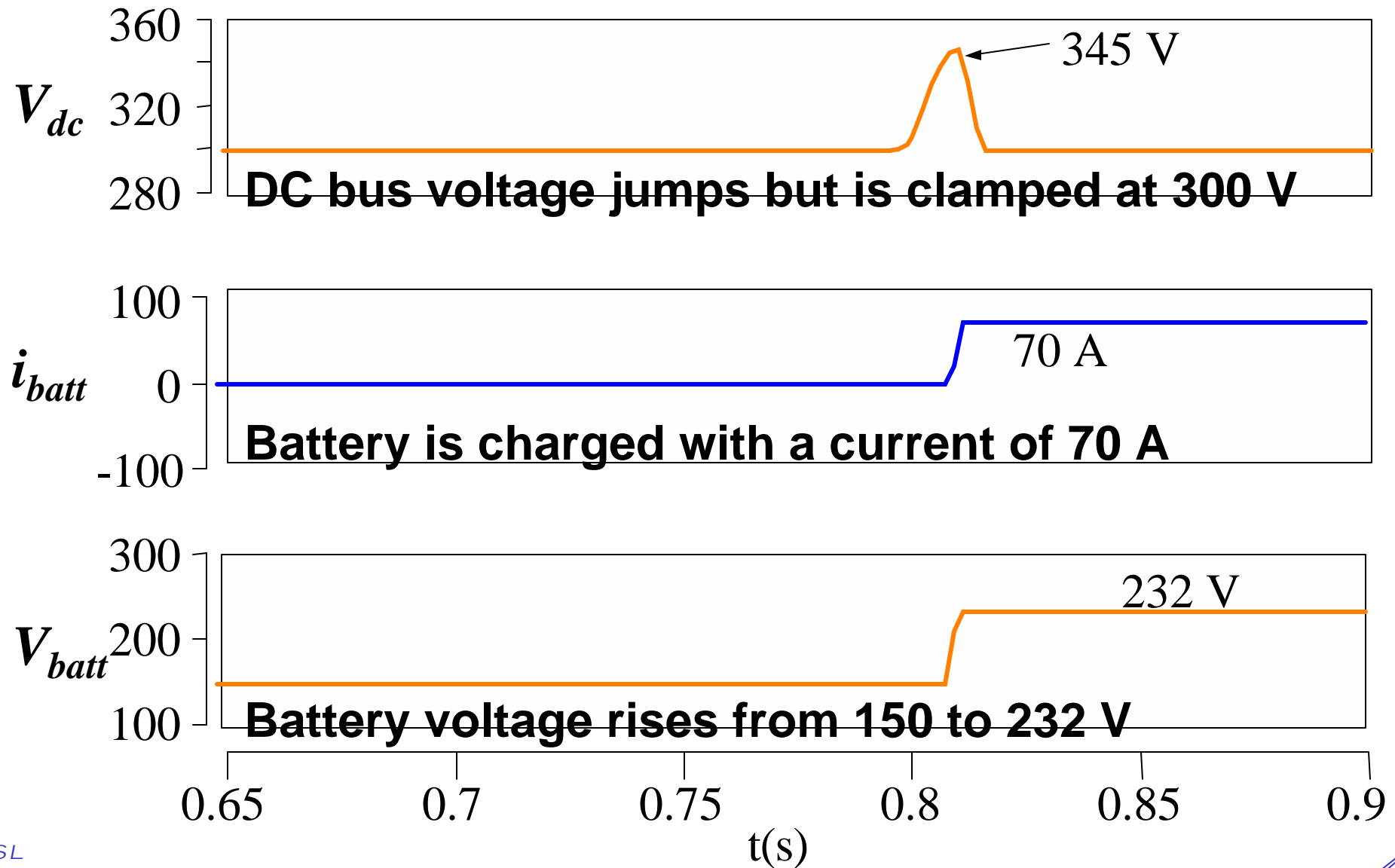
# Voltage Loop Control Response During Load Dump




# Ripple Current Cancellation with Interleaved Operation

$$V_{batt} = 190 \text{ V}, V_{dc} = 282 \text{ V}, P_o = 20 \text{ kW}$$


27-Jul-01  
17:33:24

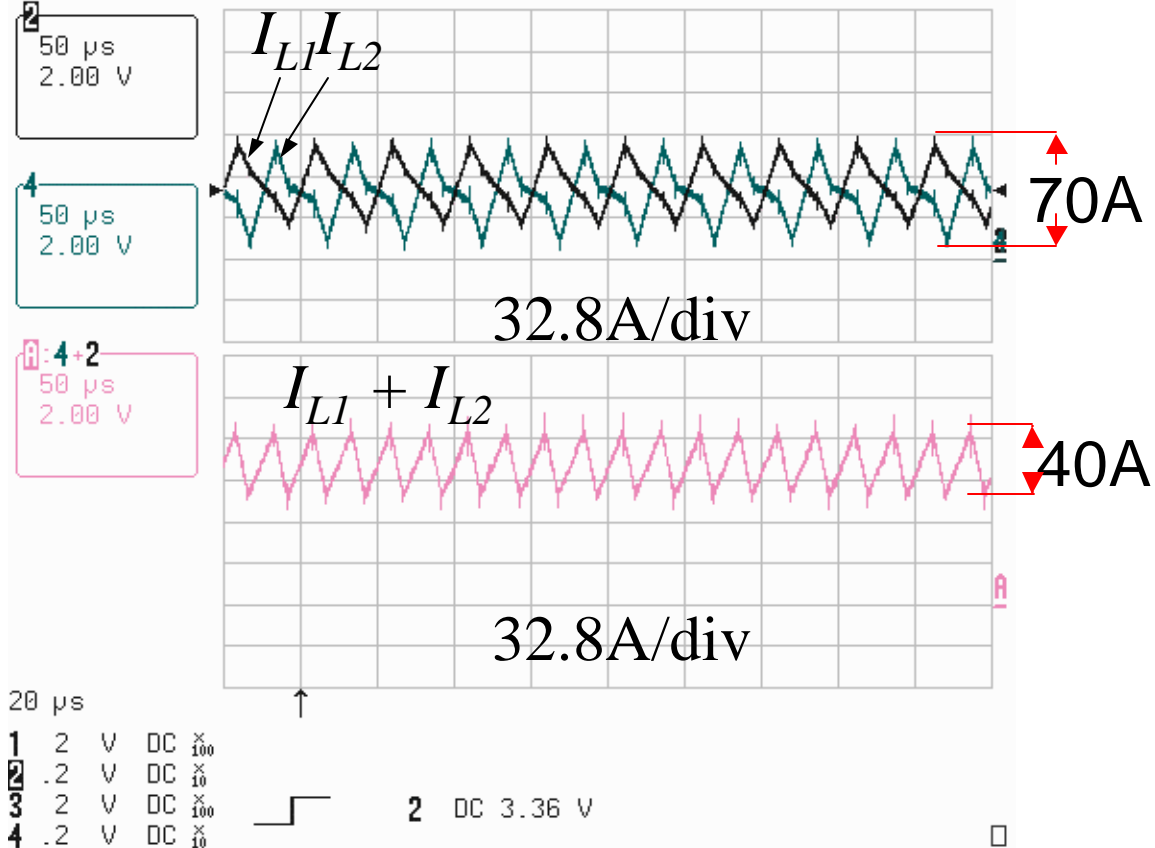

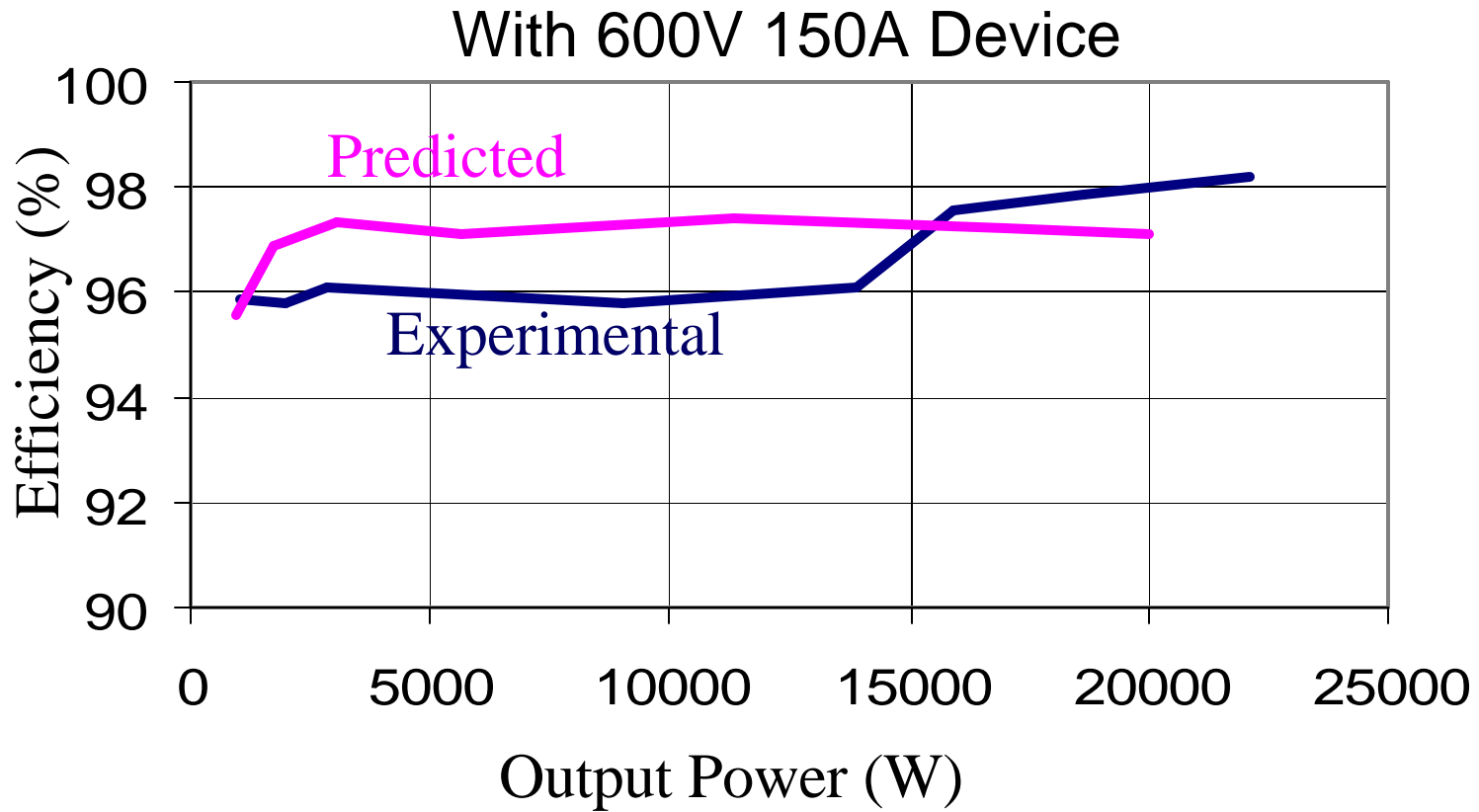
# Efficiency Evaluation Results for Boost Mode Operation


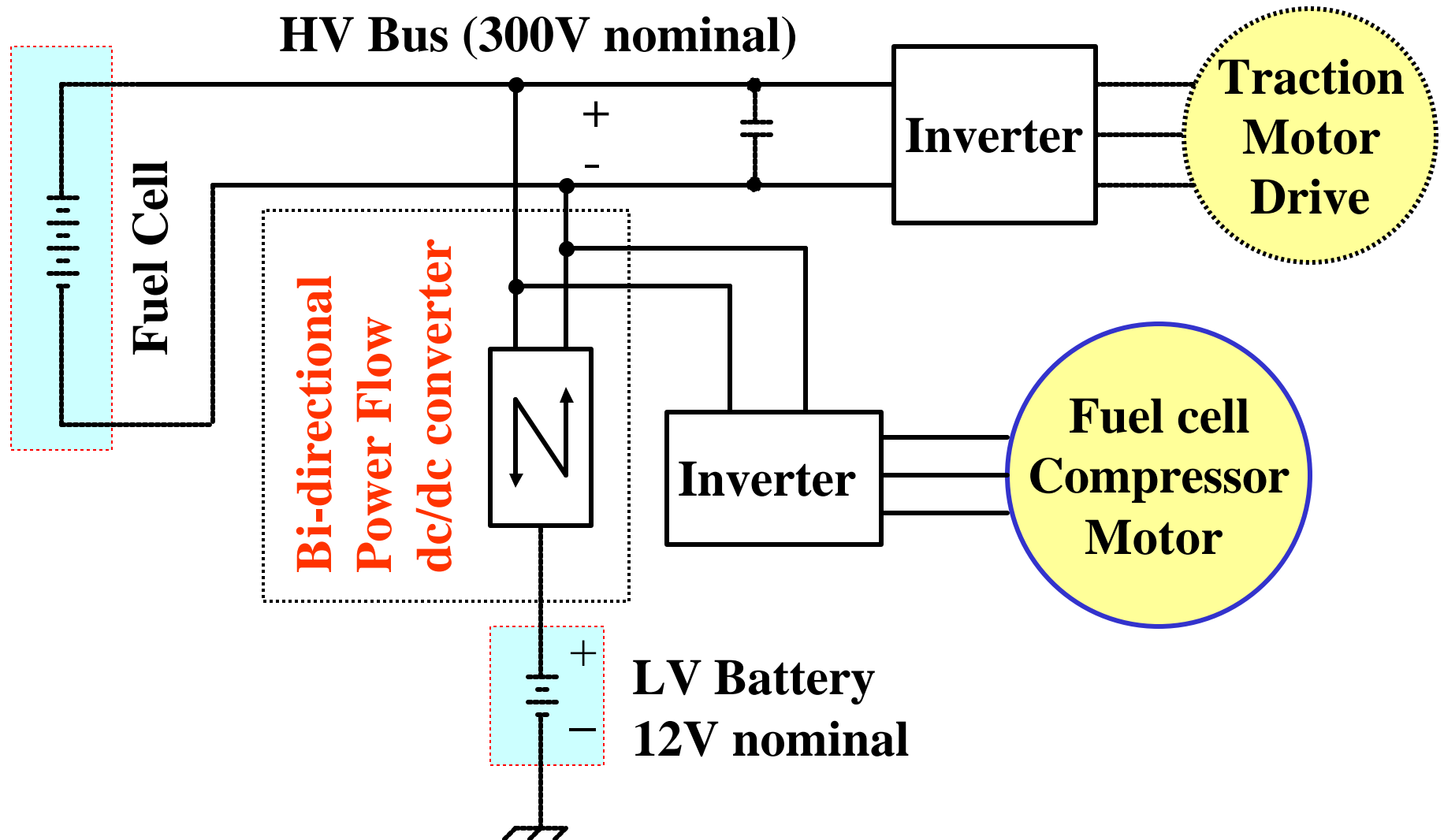
# Isolated Bidirectional DC/DC Converter for Fuel Cell Energy Management



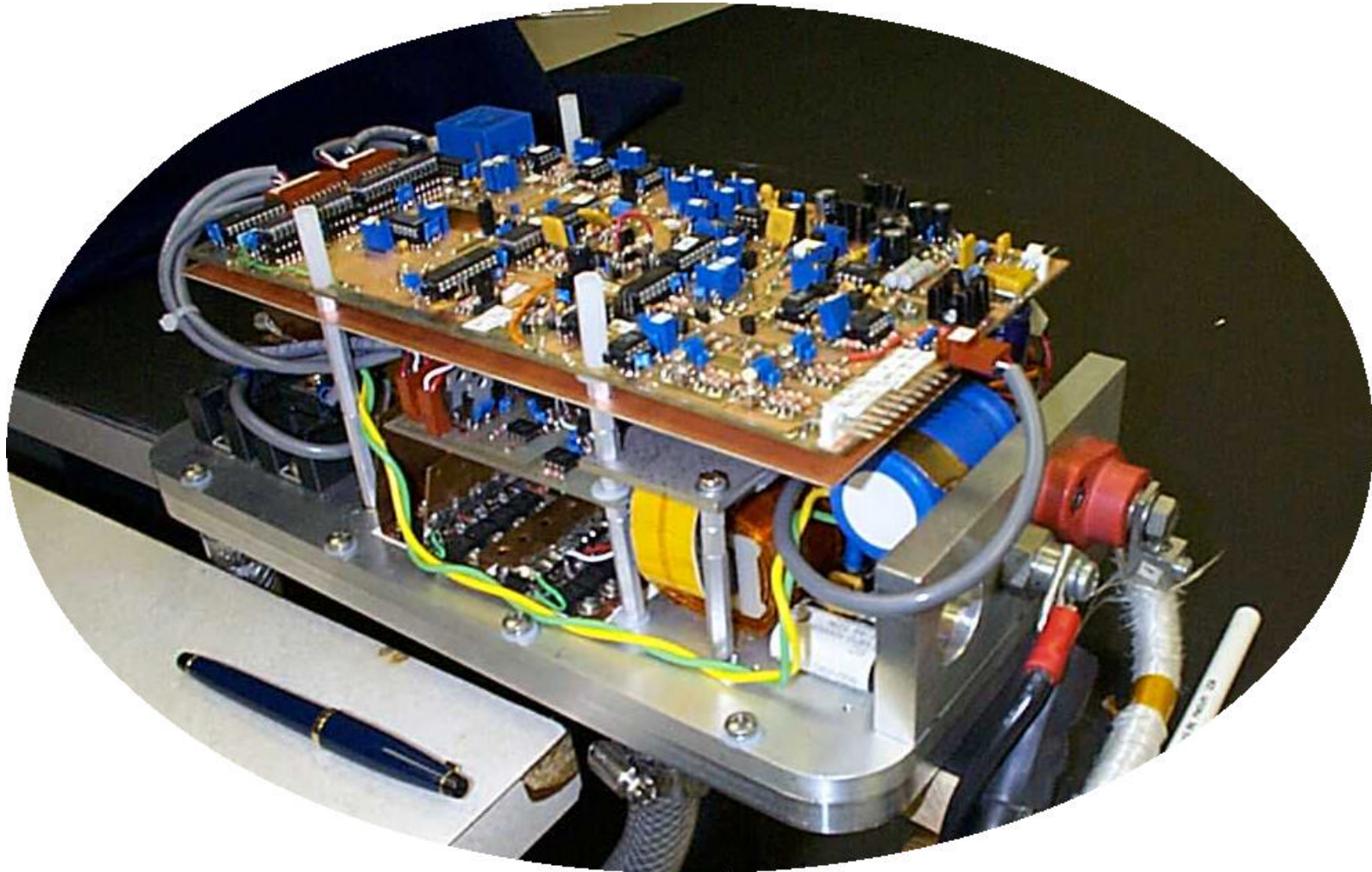
# Prototype of a Liquid Cooled 5-kW Bi-directional DC-DC Converter



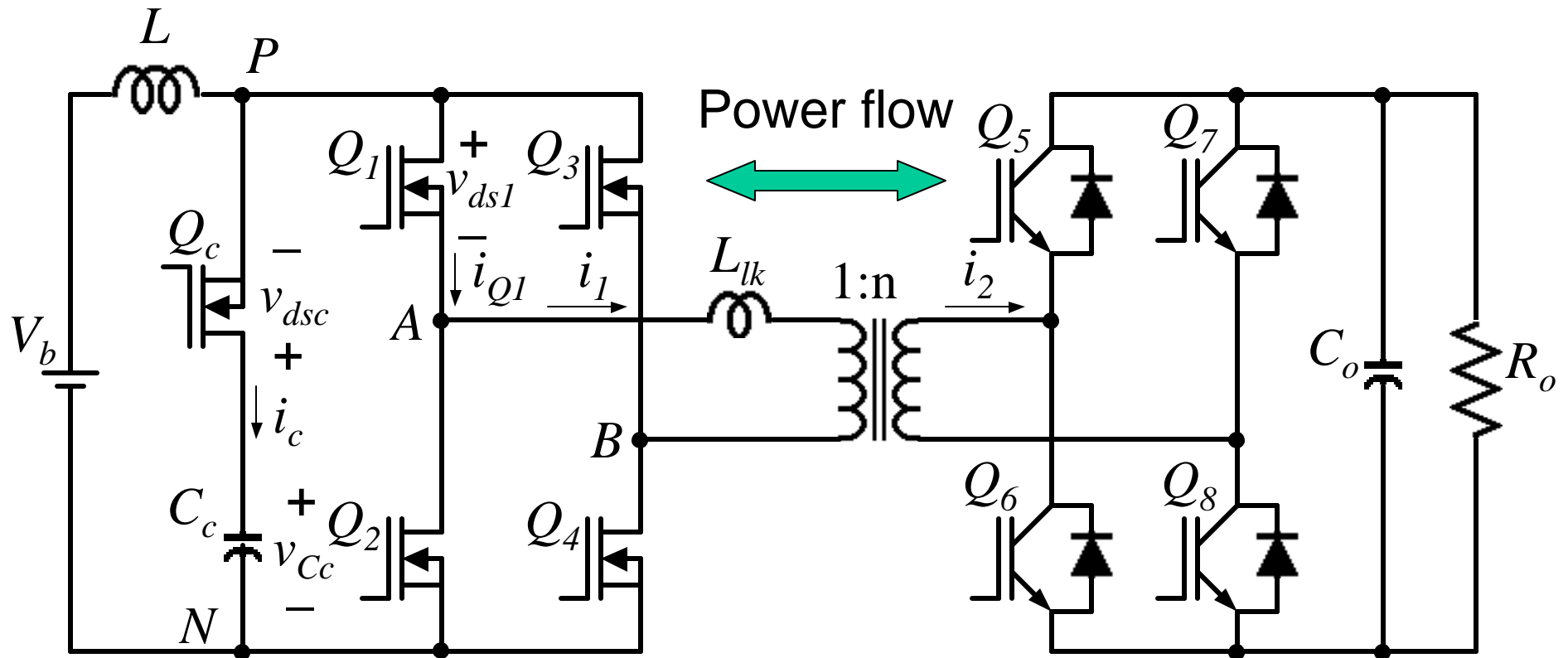
# An Isolated Bi-directional DC-DC Converter

LV-Side “Current Source” and HV-Side “Voltage Source”




- ✓ Simple voltage clamp circuit implementation
- ✓ Simple transformer winding structure and low turns ratio
- ✓ High choke ripple frequency ( $2f_s$ )
- ✗ Start-up problem


# Boost Mode Operation

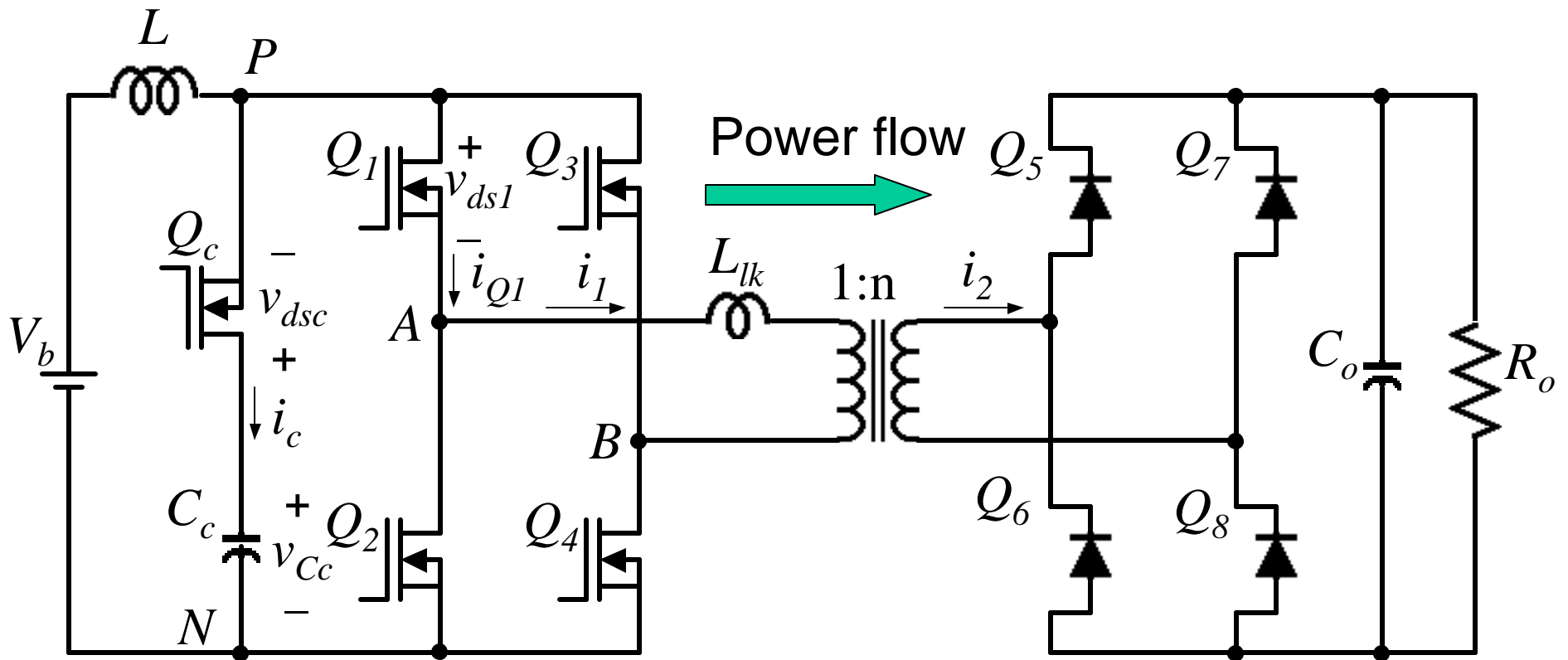

# Buck mode Operation

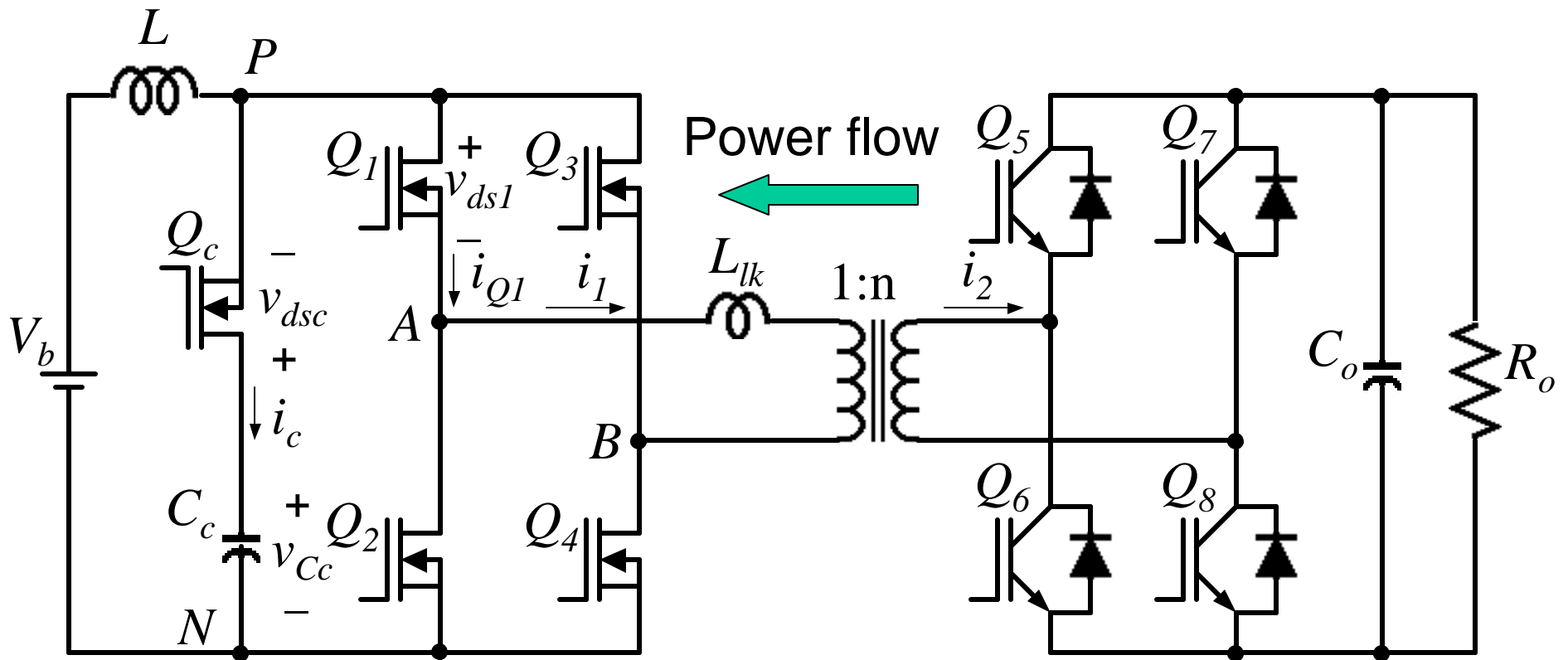

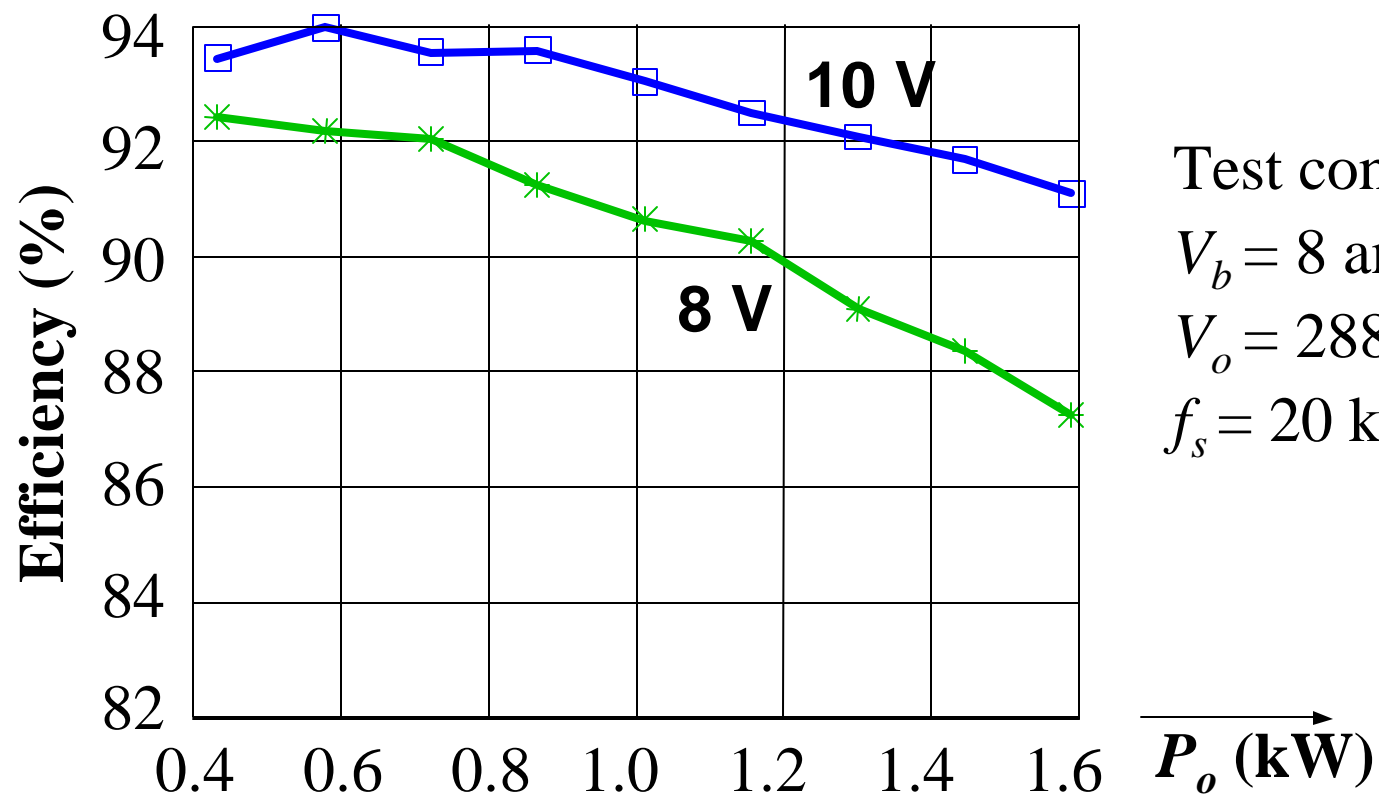
# Measured Efficiency of a Full-Bridge Boost Converter



Test conditions:  
 $V_b = 8$  and  $10\text{V}$   
 $V_o = 288\text{V}$   
 $f_s = 20\text{ kHz}$

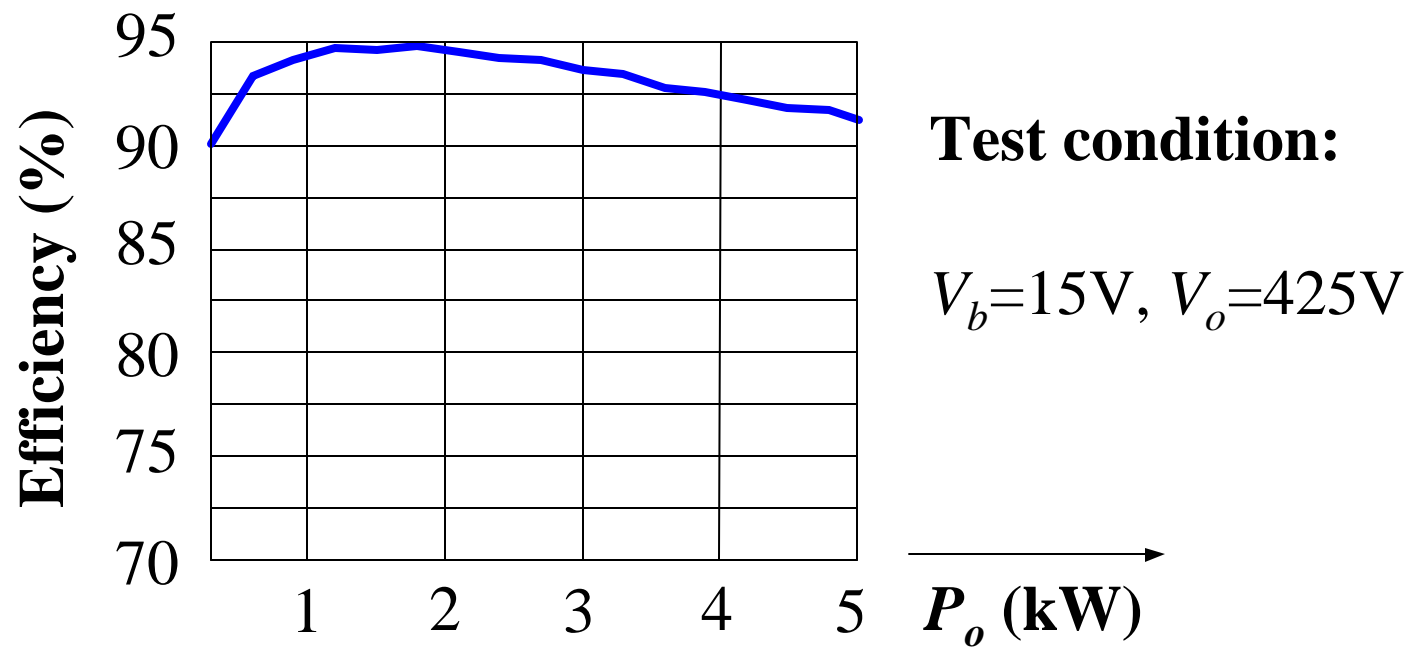
# Measured Efficiency under Buck Mode Operation



**High efficiency because**

- (1) more devices in parallel on the LV side,**
- (2) the active clamp circuit provides lossless snubbing and soft-switching operations, and**
- (3) synchronous rectification.**

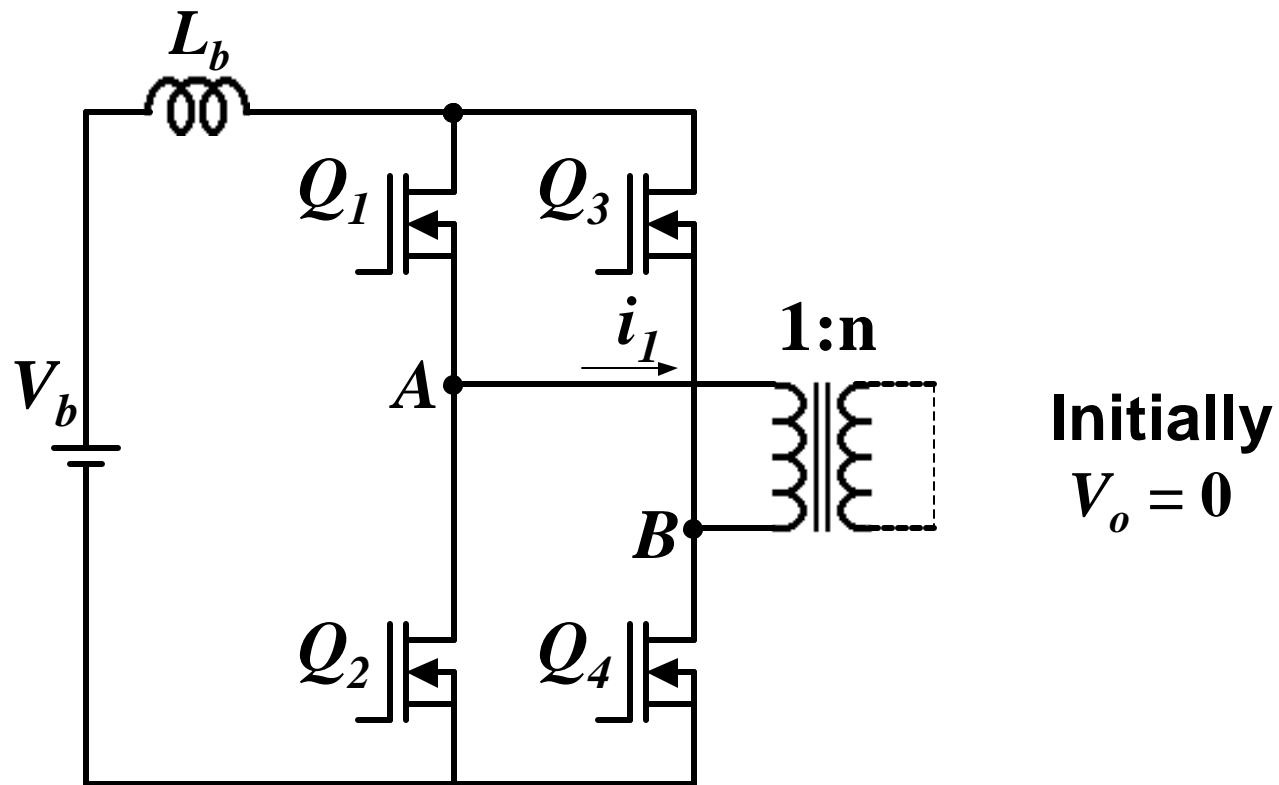
# Startup is a Problem with Isolated Boost




## During startup

- Initial output voltage is zero, or short-circuited
- Energy charged in  $L_b$  can't be transferred to secondary until  $V_o > nV_b$
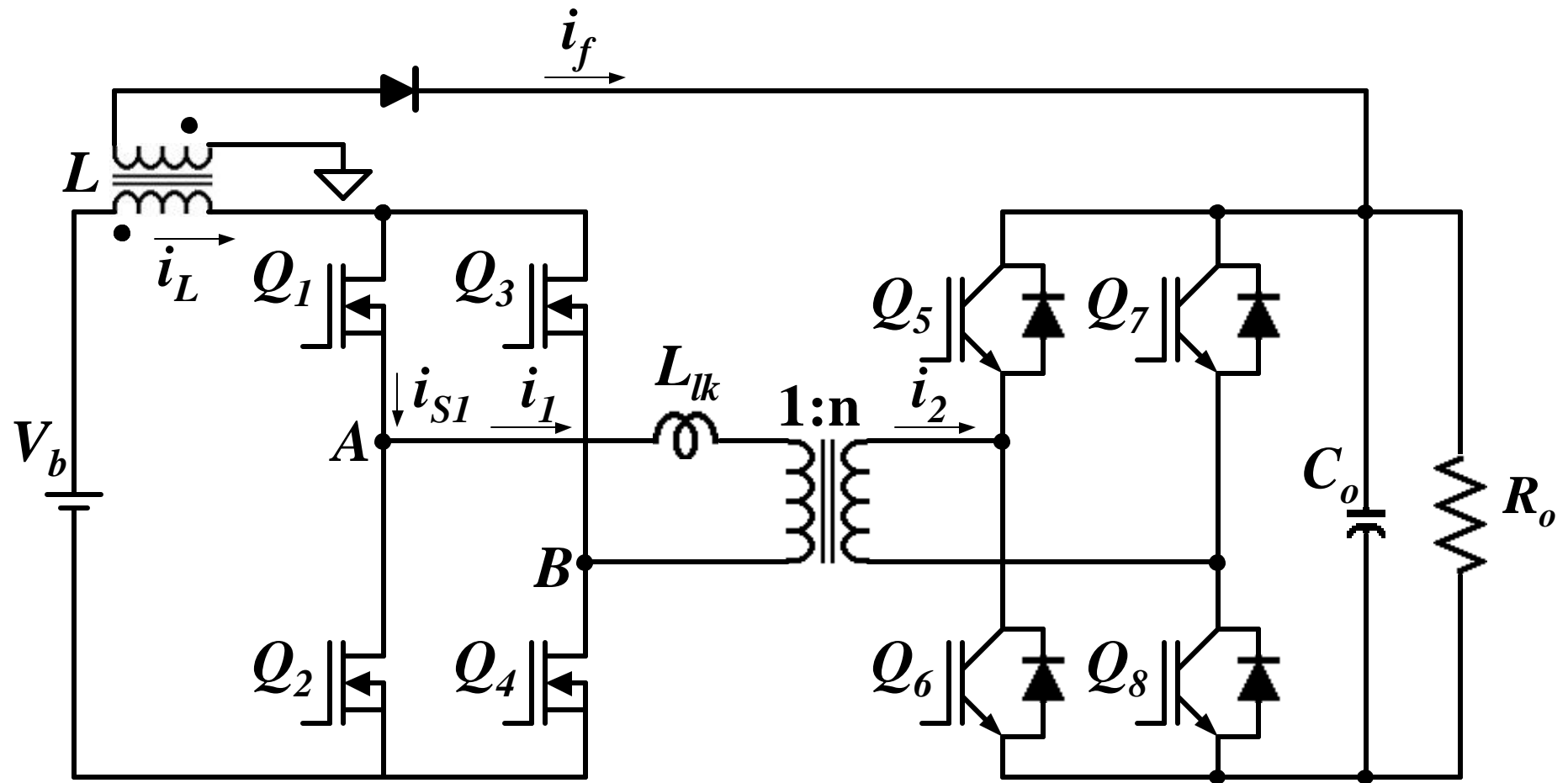
# Adding a Flyback Winding for Start-up Operation



# Start-up Operating Waveforms

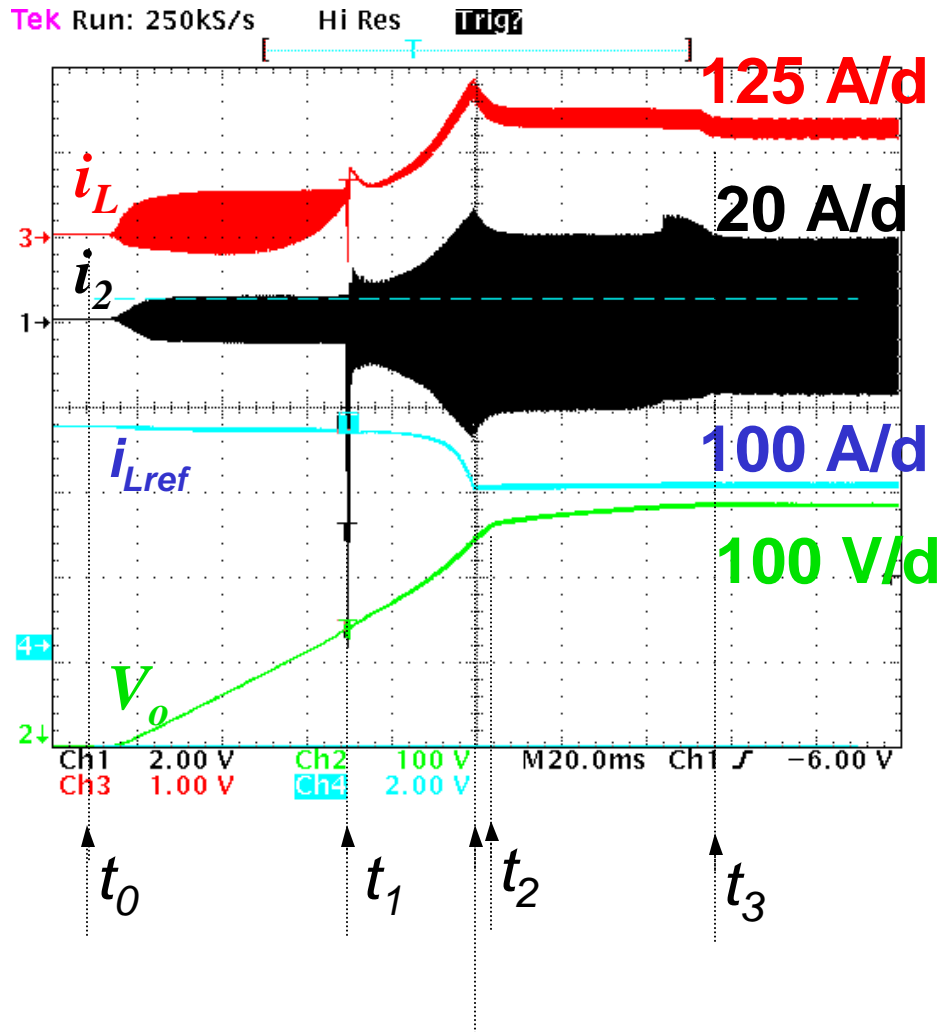

## Start Up Process:

- $t_0-t_1$  Start up mode, open loop controlled
- $t_1-t_2$  Boost mode, open loop controlled
- $t_2-t_3$  Boost mode, inner current loop regulated
- $t_3-$  Boost mode, outer voltage loop regulated

$$V_b = 12 \text{ V},$$

$$I_L = 161 \text{ A},$$

$$V_o = 280 \text{ V},$$


$$P_o = 1.83 \text{ kW}$$

Average current loop regulated


## 2001 Future Energy Challenge Inverter

- **Cost: <\$500 for 10 kW design**
- **Input: 42 to 72 V**
- **Output: 120/240 V, 60 Hz, 10 kW**
- **Size: <50 L**
- **Weight: <32 kg**
- **Efficiency: >90%**
- **THD: <5%**
- **Voltage regulation:  $\pm 6\%$**
- **Protections: voltage, current, temp., etc.**
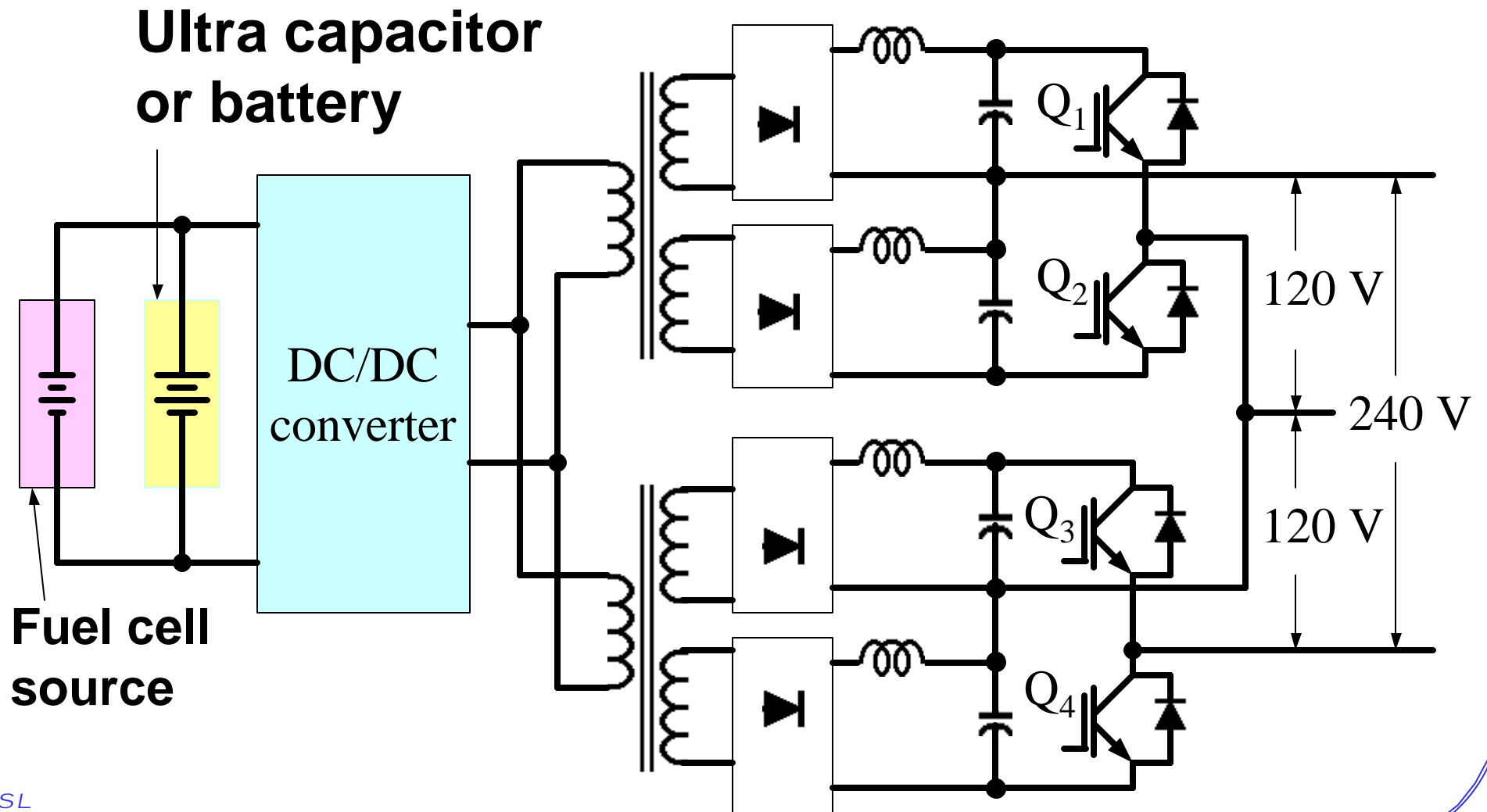
# Placement of Low Voltage Energy Storage for Energy Management


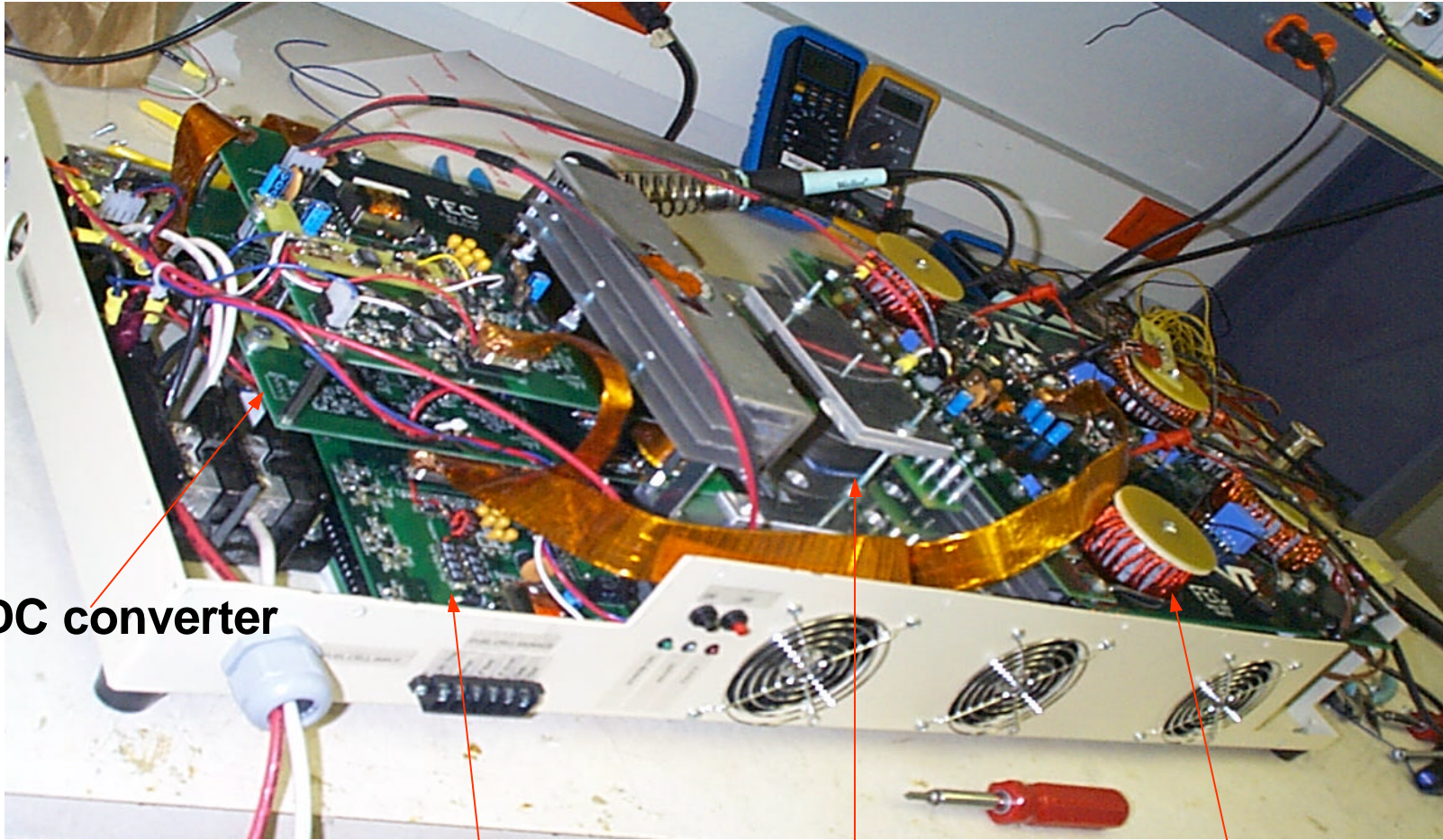
# A 10-kW Split Single-Phase Fuel Cell Inverter for Residential Applications



**DC-DC converter**


**Digital controller**

**High-frequency transformer**

**DC-AC inverter**

# Fuel Cell Voltage During Load Dump


## From 1.1 kW to 500 W

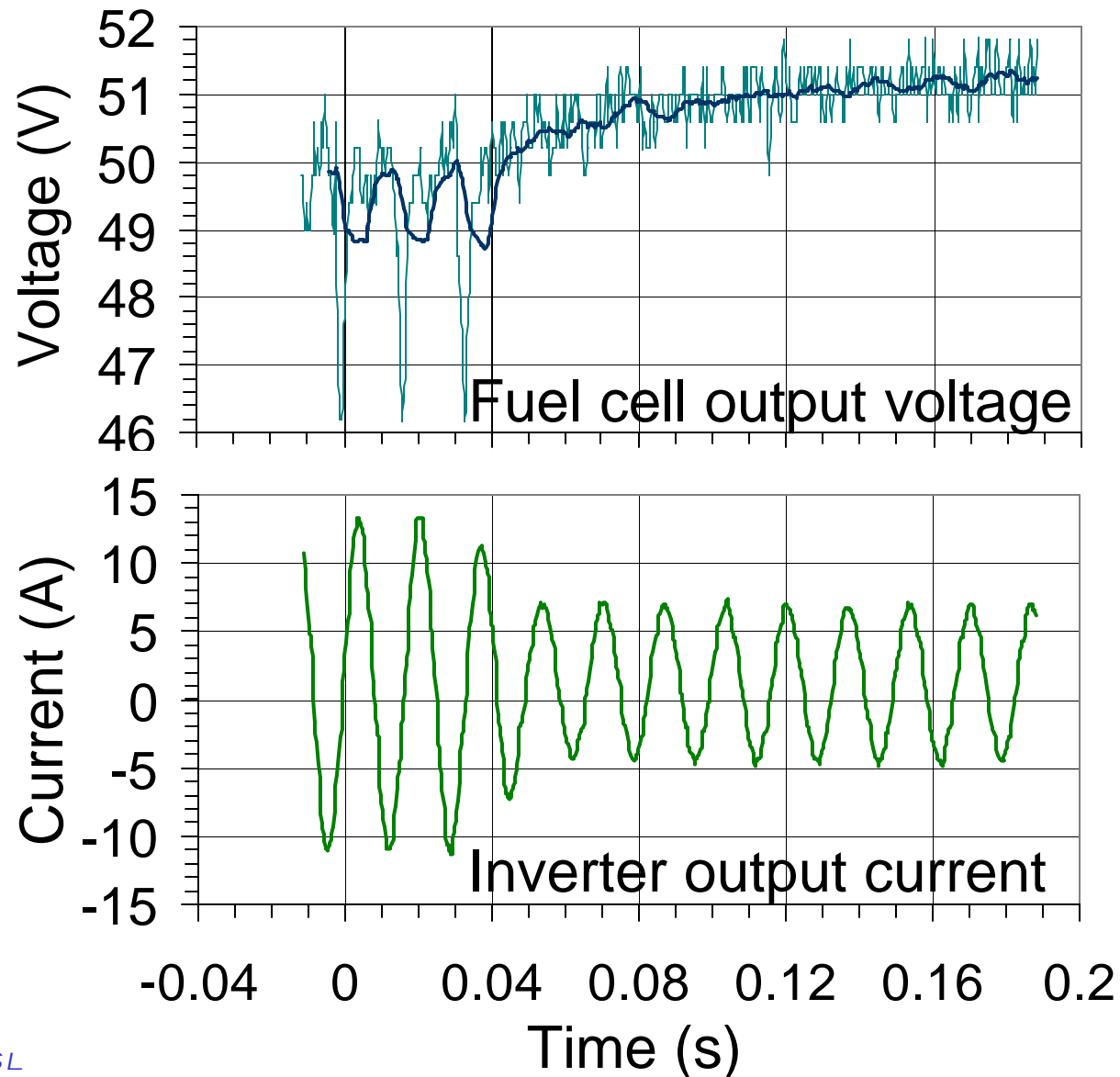

- Experiment with a 3-kW PEM fuel cell and a 3.3-F ultra capacitor.
- Use incandescent lamps as the load.
- Ultra cap smooths the load transient effectively.
- Fuel cell time constant is reasonably fast, in millisecond range.
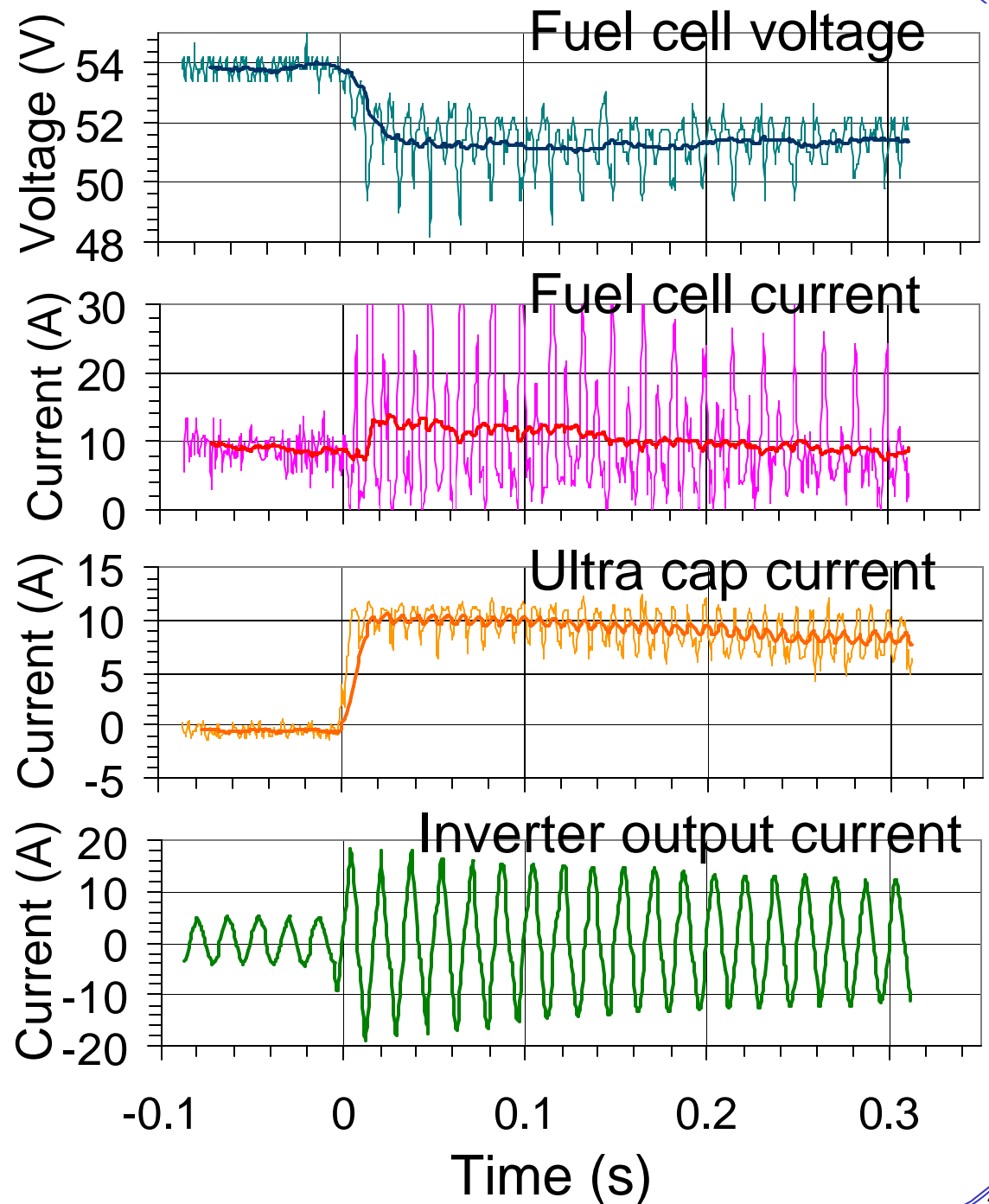
# Fuel Cell Dynamic Response During Single-Phase Motor Start-up Transients

- Ultra cap absorbs significant current during load transient
- Dynamic fuel cell input current and voltage ripples are severe



# Issues to be Discussed in Fuel Cell Power Conditioning

- Advanced **Bi-directional dc-dc converter** technologies
- High power **interleaved control** and associated technologies
- **Digital control** for high power dc-dc converters
- Fuel cell **voltage standardization**
- Fuel cell **ripple current specifications**
- Fuel cell **output voltage dynamic**
- Fuel cell and power conditioning **interface and communication protocol**
- Fuel cell system and **utility interconnection**