

*Interface & Energy Buffer
for Fuel Cell Applications
System*

Guozhu Chen

University of California Irvine

2002.8.8 NFCRC in Irvine, California

Outline:




- 1) Three interfaces of PE for FC**
- 2) Electrical characteristics of FC**
- 3) Energy Buffer (EB) concept for FC***
 - * Why EB**
 - * Functions & implement**
 - * Example & relationships**

1) A three-interface model of PE for FC

FC Stacks

Power Electronic Interface

App. Object

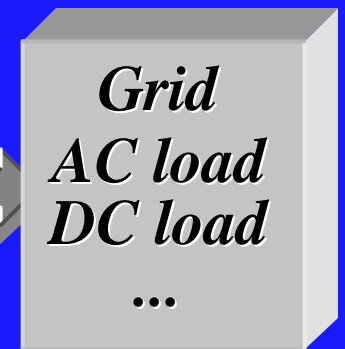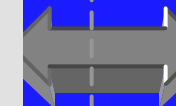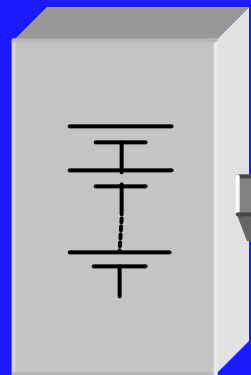



* FC app. greatly depends on PE

* FC app. is an important sub-branch of PE

* Three interfaces

{	<i>FC ~</i>	}	ö
	<i>Load/grid ~</i>		
	<i>Energy buffer ~</i>	!!	

2) Electrical characteristics of FC


*Main
Electrical
Characteristics*

- (1) **V-I**
- (2) **V-T**
- (3) **P-I (MPP)**
- (4) **Overload ability**
- (5) **Ripple tolerance**
- (6) **Response time with load**
- (7) **Warmed up time**

Steady state


Dynamic ~

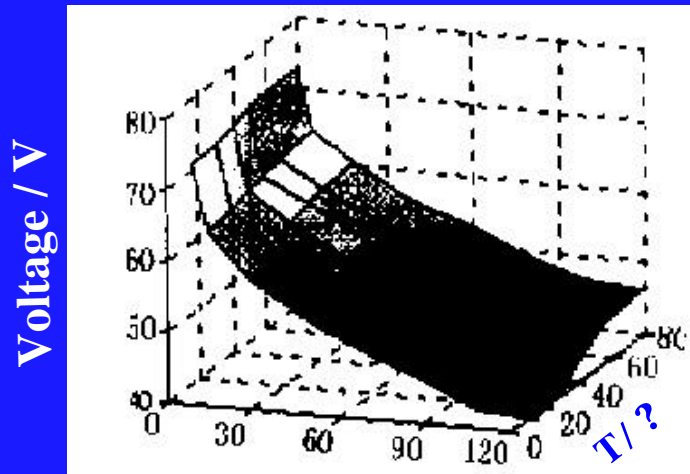Some electrical Characteristics of a 5kW (74 stacks) PEMFC



Current/A

V-I Characters at different temperature

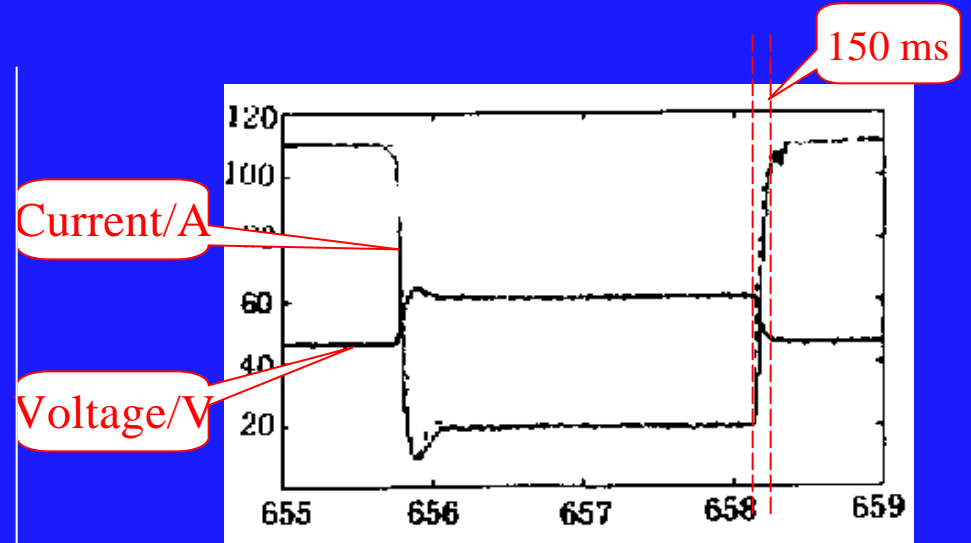


Current/A

Voltage/V

150 ms

Time/s

Dynamic load Character (78?)

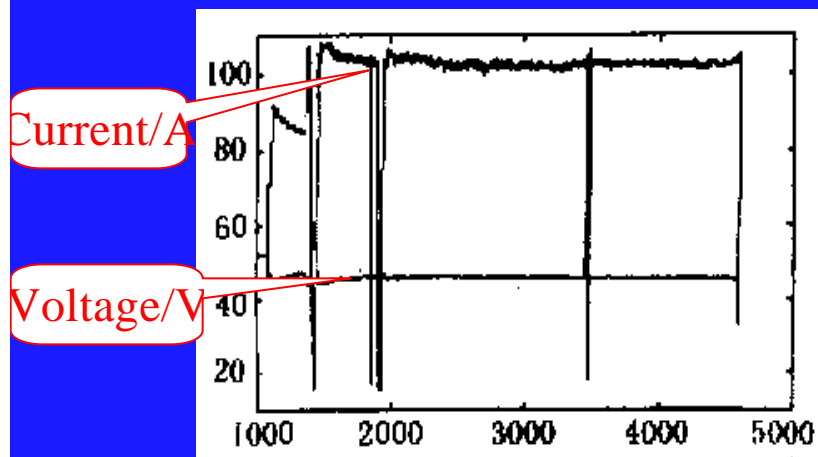


Current/A

Voltage/V

Time/s

Overload Capability (120% load)

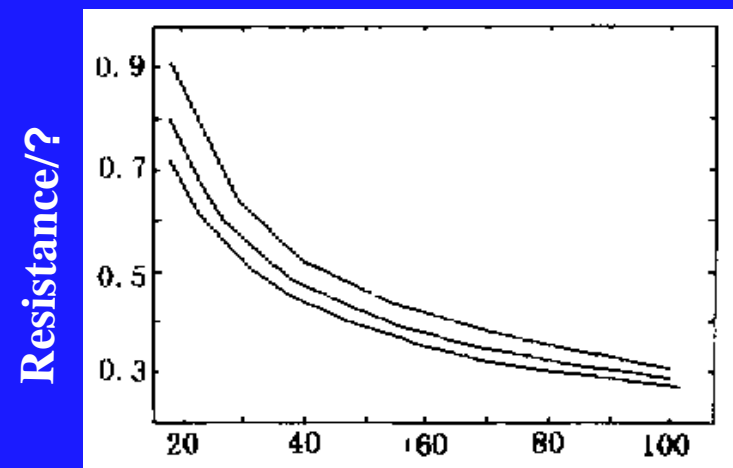

Resistance/?

Current/A

Equivalent inner resistance (15-48-78?)

3) Energy Buffer (EB) concept for FC*

** Why Energy Buffer ?*

Conflict: FC characteristics ?? Energy requirements

FC : Primary DC source (not ideal)

Goal: Convert to desirable level & forms;

*On one hand
(Fuel Cell)*

- * **Voltage variable** (with Load, Temperature, ...)
- * **Limited overload capability**
- * **Single power flow direction**
- * **Slow response:** 100 ms~s (to Load/PE device)
- * **Poor ripple tolerance**
- * **Slow warmed up:** ~tens of minutes

However, most applications are subjected to:

Current ripple:

{ Output frequency (60Hz, 120Hz, 360Hz, or variable ~)
Switching frequency (DC/AC , DC/DC)

Power flow stress:

{ Reactive load (inductive machine)


Response time:

{ Load fast change
Warmed up (e.g. vehicle)


Overload :

{ Induction motor start (5~10 times of rating)


Output Voltage/Current

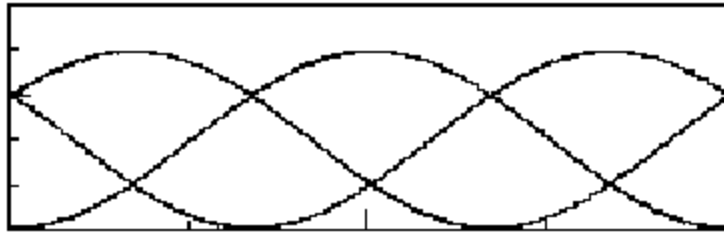


Input Current/Power

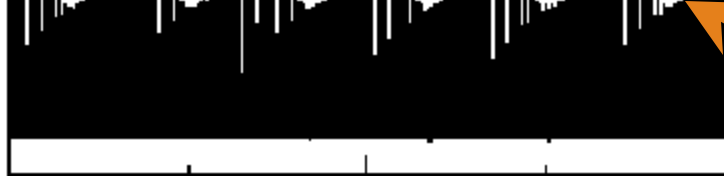

Output Current

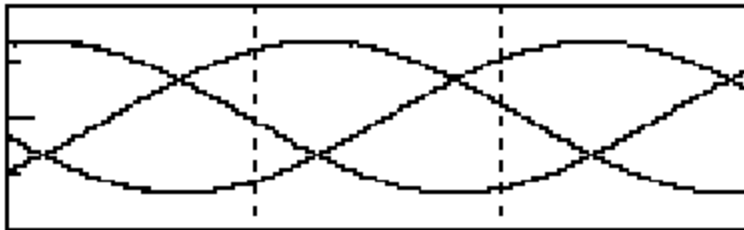

Input Current/Power

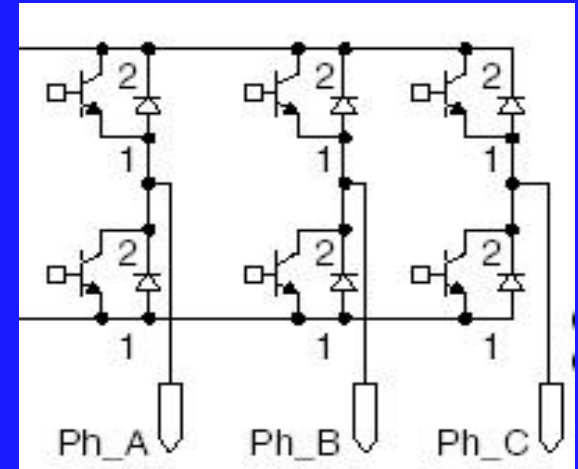





DC bus

AC Load/Grid

Grid/Resistive load

Reactive power/Current flow
(Inductive load)

Input current & power ripples of DC/AC

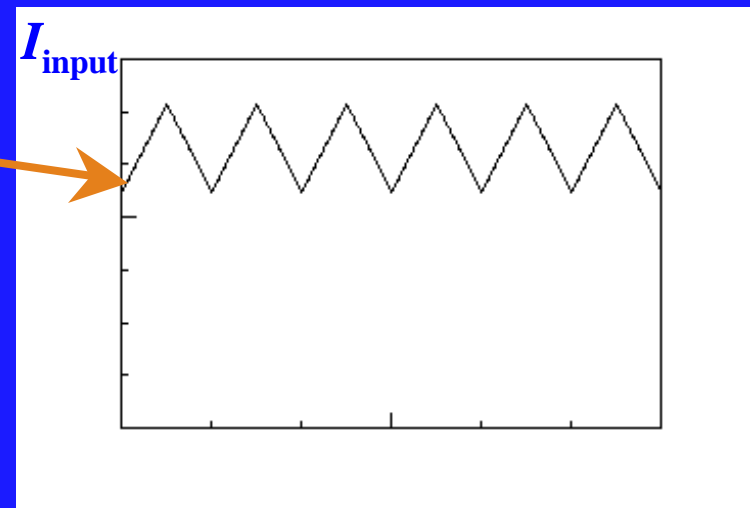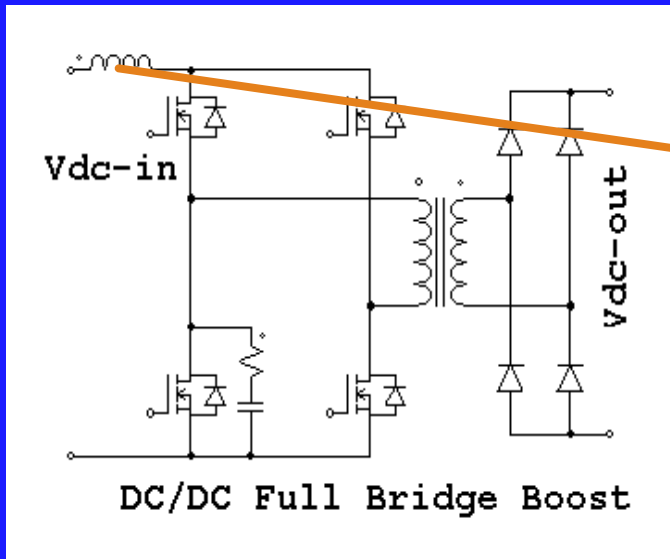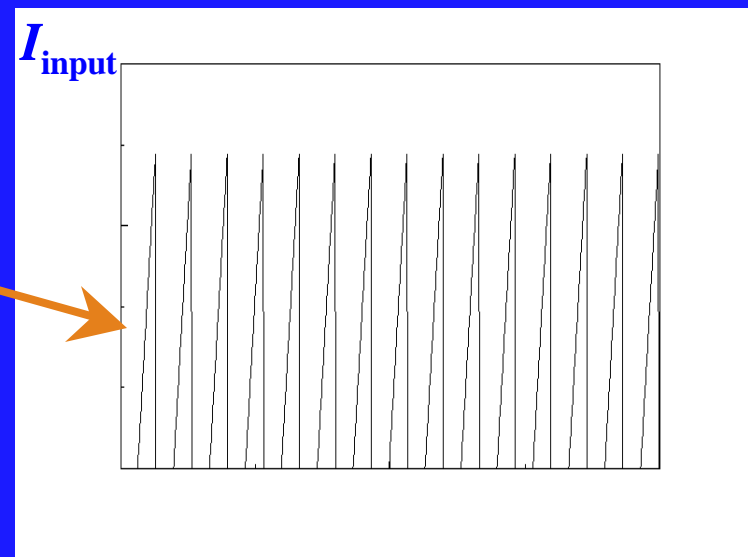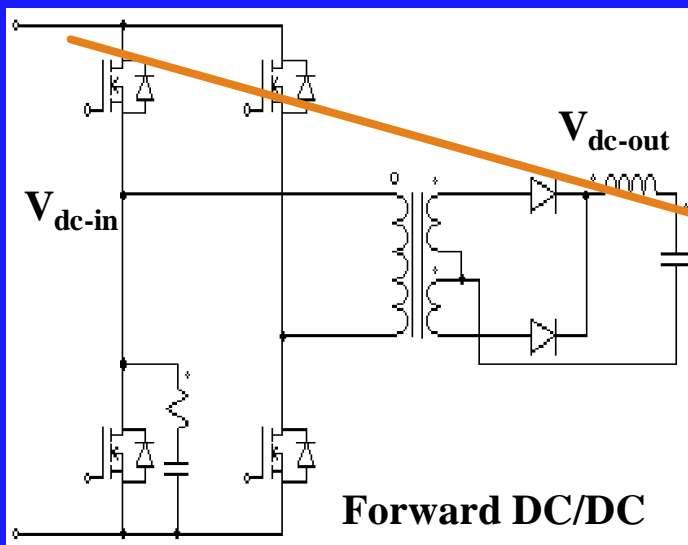

Input current & power ripples of DC/DC

**** Functions of Energy Buffer***

- * Buffer for Current Ripple**
- * Sink for Reactive/Regenerative Power** (from load)
- * Storage for over-produced power** (from FC)
- * Provide Overload/Peak Current**
- * Provide Warm up power**

** Implement methods of Energy Buffer*

- * Capacitor
- * Super-Capacitor
- * Flywheel
- * Super-inductor
- * Battery
- * Pumping Generator station
- * Rechargeable “Fuel Cell’s device”

Fast response time

Medium term/energy

;

;

Long term, larger Energy

Low efficiency


Promising EB trend!

High efficiency/power

Smaller size

Practical: C+SC or C + Battery

*** Example of EB for Vehicle Driver :**

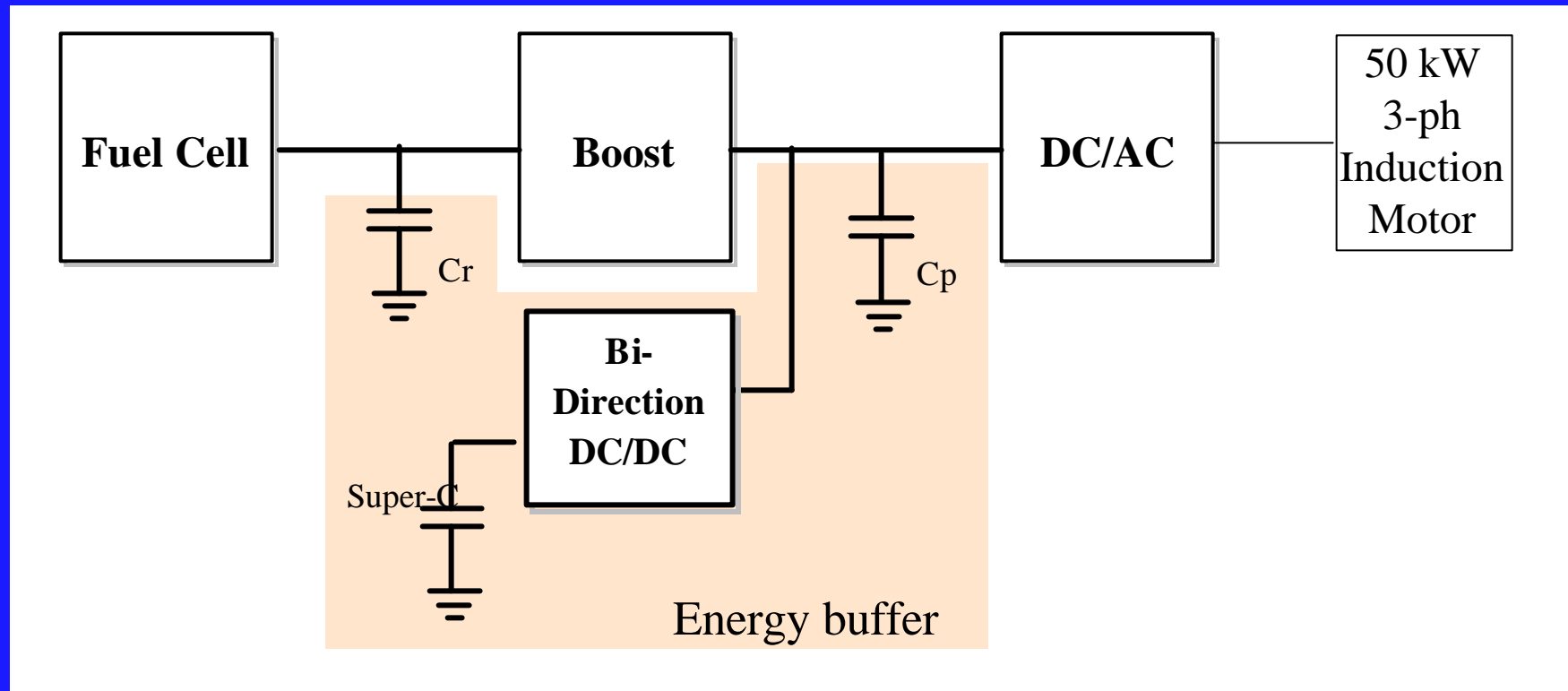

C_r

- SW frequency ripple


Super C

- Long term energy buffer
- Warm up

C_p

- SW frequency ripple
- Output frequency ripple
- Peak power (5~ times)
- Reactive power flow
- Fast load transient buffer

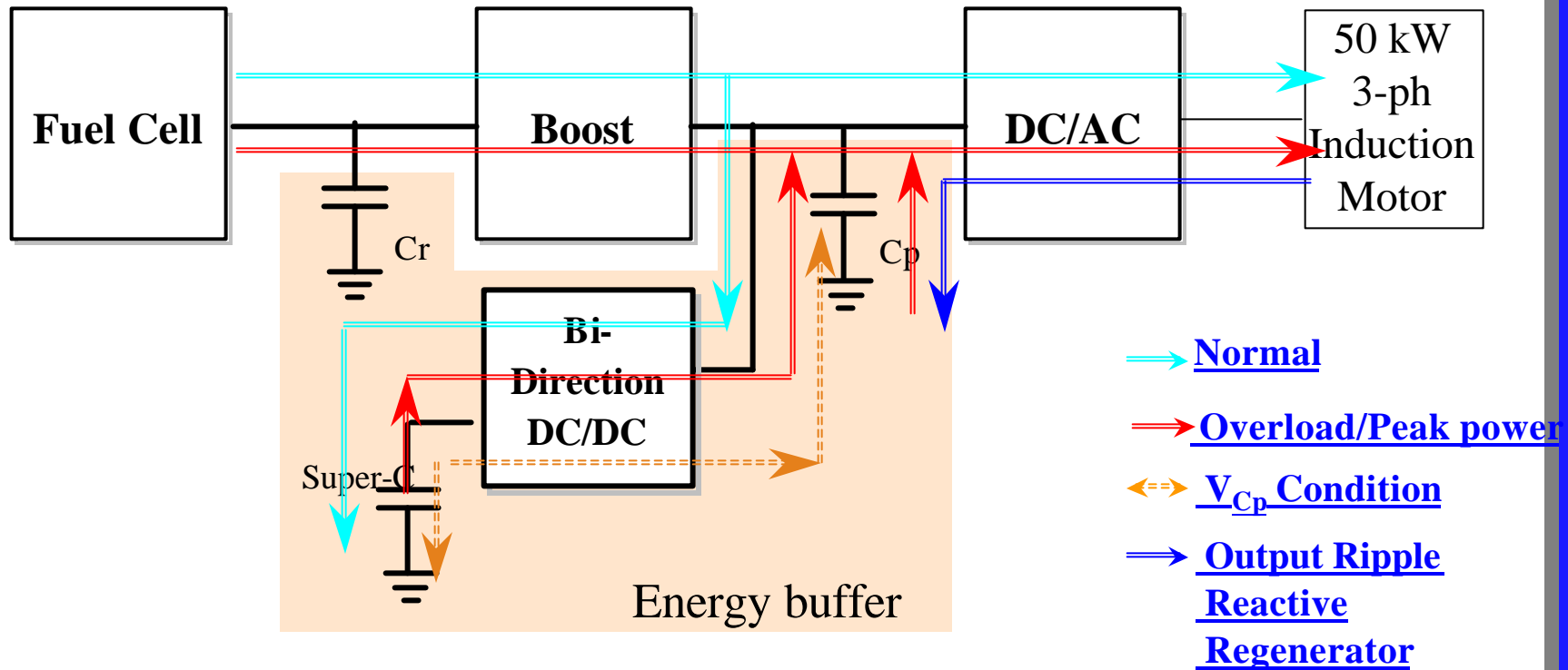
** Power flows in different operation states :*



* *Some relationships of the Example:*

? DC/DC SW Ripple filter
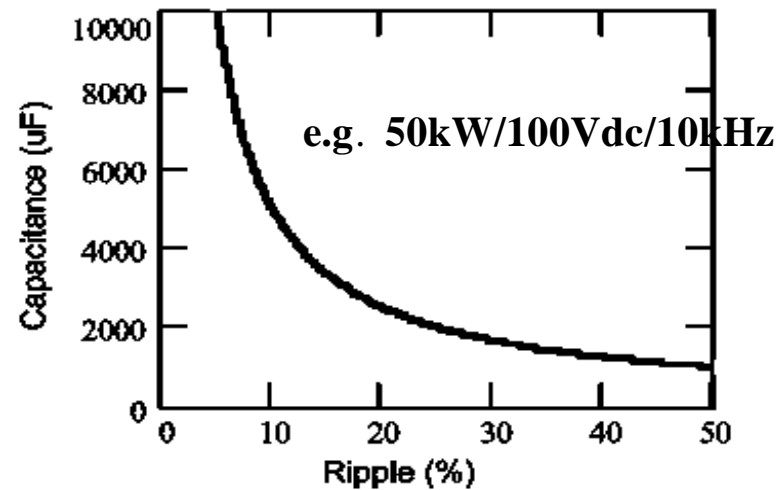
$$C_r = \frac{I_{(peak, max)}}{\Delta V \cdot f_s}$$



? DC/AC Energy Buffer C_p

$$C_p \geq I_{pk} / (f_{out} \cdot \Delta V)$$

$$C_p \geq (1 - \sin 60^\circ) I_{pk} / (6 f_{out} \cdot \Delta V)$$

$$C_p \geq (n - 2) P \cdot T_{overload} / (\Delta V \cdot V_{dc2})$$


$$C_p \geq P \cdot \sin \mathbf{q} \cdot (\mathbf{q} / 2\mathbf{p}) / (f_{out} \cdot \Delta V \cdot V_{dc2})$$

$$C_p \geq P \cdot \Delta T / (\Delta V \cdot V_{dc2})$$

Max(C_p)

- SW f ripple
- Output f ripple
- Peak power (5~ times)
- Reactive power flow
- Fast load transient buffer

Super-Capacitor-Large Energy Buffer

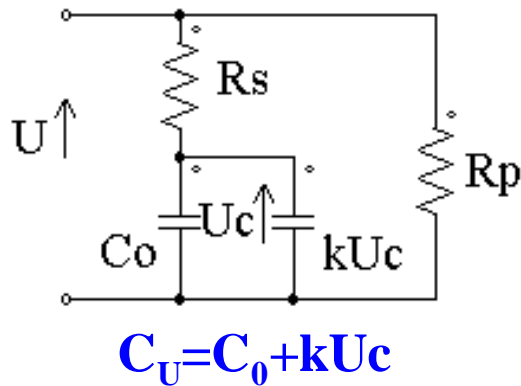

e.g.	2600F/2.5V/100A	
	C_0	1800F
	k	340F/V
	R_s	0.8 m?
	R_p	3 k?

Characteristics:

- Larger variable capacitance
- Small leakage current
- Long Energy storage time
- High reusable energy rate

$$\sim 10^3 \text{ F}, \quad i = (C_0 + 2kU_c) \frac{dU_c}{dt}$$

nA/mA (large arrays)

>10 days

$$80\% \text{ E @ } 50\% \text{ V} \quad \Delta E = \frac{3}{4} E(U_c) + \frac{1}{12} kU_c^3$$

- Long response time & limited current Charge/discharge needed !


Energy stored in Super C: ~2000F@50V

? 50s for 50kW load

? 100Ah/12V Battery


$$\text{(60\% discharge } \frac{1}{2} C(U_{c1}) \cdot (U_{c1}^2 - U_{c2}^2) = \int v i dt \approx \bar{V} \cdot \bar{I} \cdot T \times 3600)$$

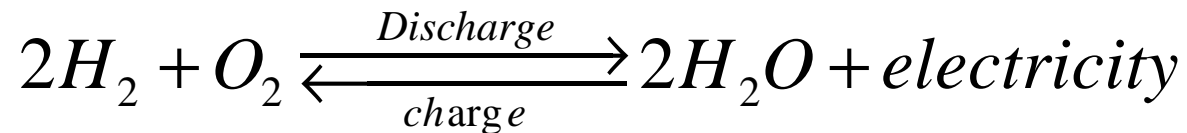“Rechargeable Fuel Cell’s device” is a desirable & Promising Energy Buffer for high power application (~500MW)!



Conclusion

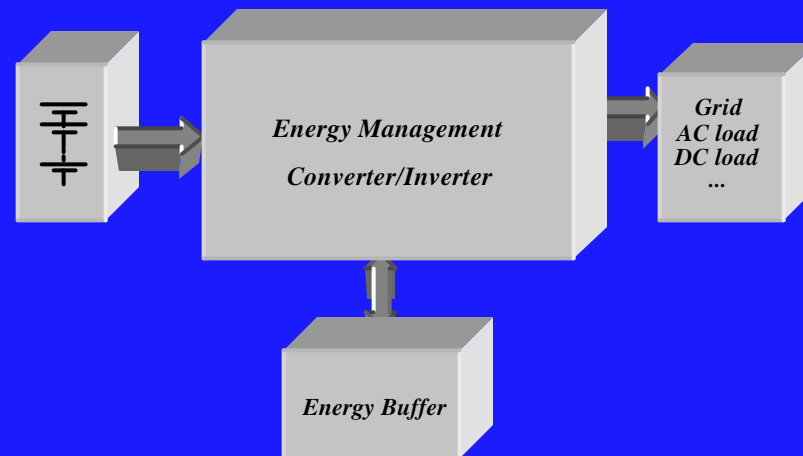- * *EB is an important interface of FC's application*
- * *Functions & Implements of EB are discussed*
- * *Relationships of EB based on an example are derived*



Thanks!

